

CHAPTER 5 ELECTRIC CURRENTS

Page 135,136 Ex 5.1

1. C
2. A
3. B
4. B
5. A
6. B
7. a) electrons b) Na^+ and Cl^-
8. a) collisions with the crystal lattice atoms b) collisions with lattice atoms transfers energy.
9. 0.2Ω
10. $5.0 \times 10^{-3} \text{ A}$
11. 1.35 V
12. 280 m
13. 50 m
14. Electrons drift through the lattice, as temperature increases the lattice atoms vibrate more and this increases the probability of collision and hence resistance to electrons has increased.
15. 7200 C
16. Ohmic: constant resistance, I-V graph is linear through origin;
Non-ohmic: non-linear I-V graph
17.

Appliance	Power (Watt)	p.d (Volt)	Current (Ampere)	Fuse rating needed (3,5,10,13 A)
Digital clock	4	240	1.7 102	3
Television	200	240	0.83	3
Hair dryer	550	110	5	10
Iron	920	230	4	5 or 10
Kettle	2400	240	10	13
18. 23 cents
19. 9.3°C
20. \$2.86
21. $1.5 \times 10^{-6} \text{ J}$
22. $2.5 \times 10^3 \text{ eV}$.

CHAPTER 5 ELECTRIC CURRENTS

Page 147-151 Ex 5.2

1. A
2. D
3. C
4. D
5. A
6. B
7. C
8. A. ($1/R = 1/3 + 1/3 + 1/3 = 3/3$ $R = 1\Omega$)
9. B. ($W = qV$ $V = 18J / 2 C = 9.0 V$)
10. C. (One ampere is defined as the current flowing in 2 infinitely-long wires of negligible cross-sectional area separated by a distance of one metre in a vacuum that results in a force of exactly $2 \times 10^{-7} N$ per metre of length in each wire).
11. C. ($P = VI$. If the voltage is constant, power is directly proportional to the current).
12. A. (Closing the switch will create a short-circuit, and the electrons will by-pass lamp 2, other lamps will then be brighter).
13. C. ($1/R = 1/R_1 + 1/R_2$ $1/R = R_2 + R_1 / R_1 R_2$ $R = R_1 R_2 / R_1 + R_2$)
14. B. ($V_1 = I_1 R_1 = (100) (2.2 \times 10^{-3}) = 0.22 V$
 $V_2 = I_2 R_2 = (150) (1.5 \times 10^{-3}) = 0.225 V$
 $V_1 = -I_1 r + \varepsilon$ $0.22 = -(2.2 \times 10^{-3}) r + \varepsilon$
 $V_2 = -I_2 r + \varepsilon$ $0.225 = -(1.5 \times 10^{-3}) r + \varepsilon$
 Subtracting equations $-0.005 = -(0.7 \times 10^{-3}) r$
 $r = 7.143 \Omega$)
15. C. ($V = IR = 12 / 6 = 2A$)
16. C. ($1/R = 1/4 + 1/4 = 2/4$ $R = 2 \Omega$ $R_{\text{eff}} = 2 + 3 = 5\Omega$
 $I = 15 / 5 = 3A$ V in 3Ω resistor $= 3\Omega \times 3A = 9V$
 Therefore, voltage across XY $= 15 - 9 = 6V$)
17. a) 22Ω b) 2Ω
18. $2.9 \times 10^3 J$
19. a) 24.4Ω b) $0.5 A$ c) $10 V$ d) $1.2 V$ e) $0.3 A$
20. 4.7Ω
21. When a dry cell goes “flat” its internal resistance has become large. Therefore it can’t really charge it. NiCad batteries have a very low internal resistance. Also dry cell chemistry is not reversible.
22. a) $1.54 V$ b) 0.74Ω .


CHAPTER 5 ELECTRIC CURRENTS

23. $I = \Delta q / \Delta t = (2.40 \times 10^3 \text{ C}) / (3.0 \text{ min}) (60 \text{ s.min}^{-1}) = 13.3 \text{ A}$.
The current flowing is 13A.
24. $V = IR$ $R = V / I$ $R = (240 \text{ V}) / (6.0 \text{ A}) = 40 \Omega$.
The resistance of the iron is $4.0 \times 10^1 \Omega$.
25. (a) $P = V.I$ $I = P / V$ $I = 2.5 \times 10^3 \text{ J} / 240 \text{ V} = 10.4 \text{ A}$
The current drawn is $1.0 \times 10^1 \text{ A}$.
(b) $W = V.I.t = (240 \text{ V}) . (10.4 \text{ A}) . (7.2 . 10^3 \text{ s}) = 1.8 \times 10^7 \text{ J}$
The energy consumed is $1.8 \times 10^7 \text{ J}$.
26. Energy consumed = power . time = $2.5 \text{ kW} \times 8 \text{ h} = 20 \text{ kW.h}$
Cost = $(20 \text{ kW.h}) \times \$0.14 = \$2.4$. The cost to run the heater is two dollars forty cents.
27. (i) Voltage in bottom arm is 100 V
 $V = IR$ $100 = I (1.0 \Omega + 3.0 \Omega)$ Current in bottom arm $I = 25 \text{ A}$. The current entering the top arm = $35 - 25 = 10 \text{ A}$
Voltage in 4.0Ω resistor = $IR = 10 \text{ A} \times 4.0 \Omega = 40 \text{ V}$
Voltage in R and 24.0Ω resistor = $100 - 40 \text{ V} = 60 \text{ V}$
The current in the 24.0Ω resistor = $V / R = 60 / 24 = 2.5 \text{ A}$
Current in R = $10 - 2.5 \text{ A} = 7.5 \text{ A}$
 $R = V / I = 60 \text{ V} / 7.5 \text{ A} = 8.0 \Omega$
(ii) $40 \text{ V} - 25 \text{ V} = 15 \text{ V}$
28. (i) 12 V means that it requires 12 J of energy to move 1 coulomb of charge between two points.
(ii) $\varepsilon = IR + Ir$ $14 = 12 + 5r$ $r = 0.4 \Omega$

29. (a)

$R \pm 0.5 \Omega$	$I \pm 0.1 \text{ A}$	$1 / I \text{ A}^{-1}$
2.0	5.0	0.20
6.0	1.7	0.59
12	0.83	1.2
16	0.63	1.6
18	0.56	1.8

CHAPTER 5 ELECTRIC CURRENTS

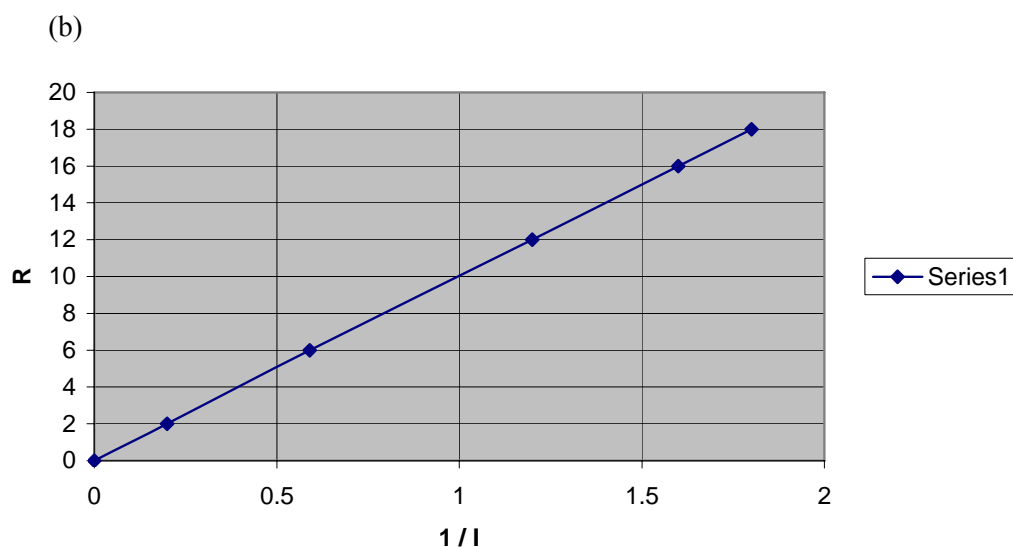

(c) the resistance is directly proportional to $1/I$ OR the resistance is inversely proportional to the current OR other correct statement

(d) the e.m.f. is the slope of the graph

$$\text{emf} = 10 / 1.0 = 10\text{V}$$

30. From the law of conservation of charge: $I = I_1 + I_2$

From the law of conservation of energy: $V = V_1 = V_2$

From Ohm's law $R = V / I$ $\therefore 1/R = I / V$

$$1/R = I_1 / V + I_2 / V \quad \text{AND} \quad V = V_1 = V_2$$

$$\therefore 1/R = I_1 / V_1 + I_2 / V_2 = 1/R_1 + 1/R_2$$

31. a) $R_{ABC} = 3\Omega$ $R_{ADC} = 1.5\Omega$

$$1/R = 1/3 + 2/3 = 1 \quad R_{AC} = 1\Omega$$

Effective resistance = $1 + 1 = 2\Omega$

(b) Total current $I = V / R_{\text{eff}} = 1.5 / 2 = 0.75\text{ A}$

Voltage in 1Ω series resistor = $(1)(0.75) = 0.75\text{ V}$

Voltage in each network = $1.5 - 0.75 = 0.75\text{ V}$

$$I_{ABC} = (0.75) / 3 = 0.25\text{ A}$$

$$I_{ADC} = 0.75 / 1.5 = 0.5\text{ A}$$

(c) $V_{AB} = (1)(0.25) = 0.25\text{ V}$

$$V_{AD} = (0.5)(0.5) = 0.25\text{ V}$$

(d) 0 V

32. Voltage in the $1\text{ k}\Omega$ resistor: $V = IR = 1000 \times 4.5 \times 10^{-3} = 4.5\text{ V}$

Therefore, voltage in the LDR = 4.5 V .

$$\text{Resistance in the LDR} = 4.5 / 4.5 \times 10^{-3} = 1000 = 1\text{ k}\Omega$$